

ELC 2137 Lab 5: Subtracting

CJ Jones, Ashlie Lackey

February 13, 2020

Summary

The purpose of this experiment was to understand how adders can be manipulated into a subtractor. Using two-full adder circuits, an additional carry in bit, or "mode" bit as called in lab, delegates if the inputs are being added or subtracted. The lab also demonstrated the primary difference between subtracting with a borrow, and adding with a carry. The addition method with the two's complement of the second number would produce a value that is not what is expected of "regular" subtraction and would have to be adjusted as such. In learning how to use the mode bit, correct subtraction was able to take place using our circuit.

Q&A

1. Why did we use two full adders instead of a half adder and a full adder?

The purpose of using two full adders was to allow for an extra carry bit that provides for the subtraction. If a half and full adder was utilized, essentially the number being subtracted couldn't have a signed bit as part of its two's complement. Therefore, the second full adder replacing the half adder allows for a "negative" number to be added to the first number.

2. How many input combinations would it take to exhaustively test the adder/subtractor?

16 input combinations would be required to exhaustively test the adder/subtractor. This can be calculated from there being 4 possible cases of each input, and each input needs to get tested against the other four inputs so, $4*4=16$.

3. Why were the combinations given in the truth table chosen?

The combinations in the truth table were picked to show the importance of a carry bit in your calculations. Without regard for the carry bit in the initial table, the results calculated under "Expected Results" were inconsistent with those found in the "Actual Results" because the expected results used addition with a two's complement with no regard for the carry bit. The circuit that was built accounts for the sign bit in the form of the "mode" being carried in to account for subtraction.

4. Do the results from your adder/subtractor match what you would expect from theory? Explain any discrepancies.

The results match what we would expect from theory, however, they differ from the initial "Expected Results". This is because the subtractor circuit accounts for the sign carry bit, while addition produces the two's complement of the result. In theory, the two's complement is sufficient as a result of subtraction using an "addition" method. However, since the circuit

cannot interpret this, it is more effective to use the subtractor method to get the exact result and not the theoretical complement.

Results

The construction of the subtractor circuit is below, along with the wiring schematic and expected results table. The "Expected Results" page documents the difference between subtraction through two's complement addition and borrow subtraction, which our results demonstrates through the "Actual Results" portion of the experiment.

 


Figure 1: Picture of the Circuit Constructed.


2/5/20

Pre-lab 4

Ashlie Lackey

2

1. Schematic of 2-bit adder

 

Ref	Des	SV	GND
X1		14	7
A1		14	7
X2		10	7
A2		14	7
X3		14	7

Figure 2: Picture of the Circuit Constructed.

Circuit Demonstration Page

Student names:

Chris JonesAsmire Larkay

Instructor Signatures

Separate Full Adders

Bob Ventresca

Two-Bit Adder

Bob Ventresca

Adder/Subtractor

Bob Ventresca

Inputs		Expected Results			Actual Results
A	B	B 2's comp	Sub	Dec	Sub
00	01	11	011	3	-1
00	10	10	010	2	-2
00	11	01	001	1	-3
01	01	11	100	-4	0
10	01	11	101	-3	1
10	00	00	110	-2	2

Figure 3: Picture of the Circuit Constructed.

Conclusion

The results of this experiment revealed the necessity of carry bits when trying to build a subtractor circuit. If you chose to use addition with the two's complement method, you would find yourself getting the wrong answer as a result of the signed result. To combat this, the most significant bit was flipped so that the correct answer was obtained as demonstrated in the Expected Results table under "Actual Results". The takeaway from this lab was the demonstration that we can manipulate tools we already have to fix other issues we are trying to solve. In this case, by combining two full adders and adding a mode bit to combat issues with signs and correct output value, we manipulated addition to work also with subtracting numbers.