

Circuit Demonstration Page

Student names: Ashlie Lackey CJ Jones

Instructor Initials

Pushbutton "Or Gate"

BB

Transistor Not gate

BB

Transistor Nor gate

BB


Transistor unknown gate

BB


Diagrams

On each of the circuits below, draw the current paths and note whether each switch, transistor, and LED is ON or OFF.

Inverter:

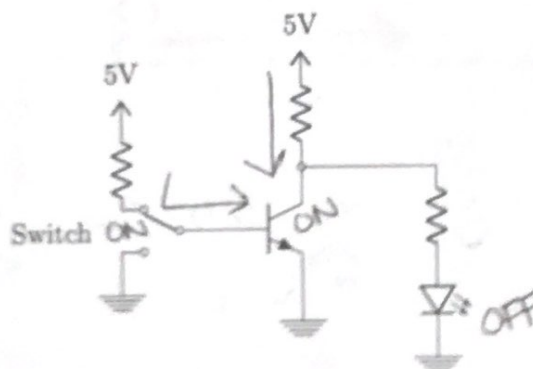

NOR:

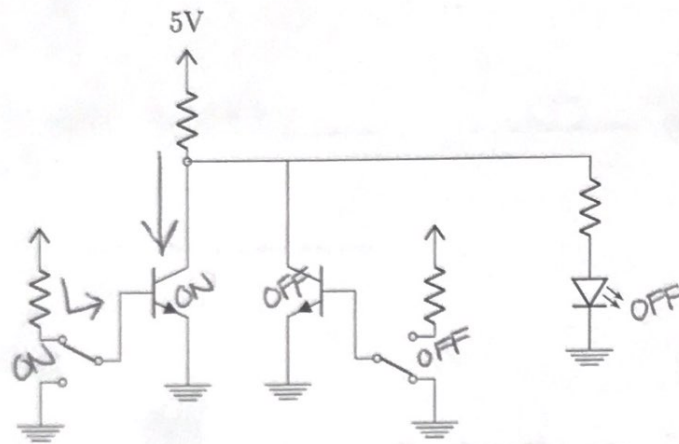

Final gate:

