

ELC 2137 Lab 5: Subtracting

CJ Jones, Ashlie Lackey

February 20, 2020

Summary

The purpose of this lab was to learn how to use the hardware description language Verilog to test digital circuits through designing and making testbenches. By coding a half-, full-, and 2-bit adder and testing them, skills in organizing files, learning syntax, and understanding gate-level code were obtained. This provides students with a basis for coding in Verilog, which will later be utilized for working with the FPGA Basys3 boards.

Q&A

1. What is one thing that you still don't understand about Verilog?

We are still confused as how to properly run testbenches, and how to look for errors when the results don't look like how they are expected to.

Results

Below are the results for running the half-, full-, and 2-bit adders. The design and testbench code for each adder is included along with each expected results table and the block diagram of each digital circuit. As the ERT's and screenshots each indicate, the results from the testbench simulations do match what is expected.

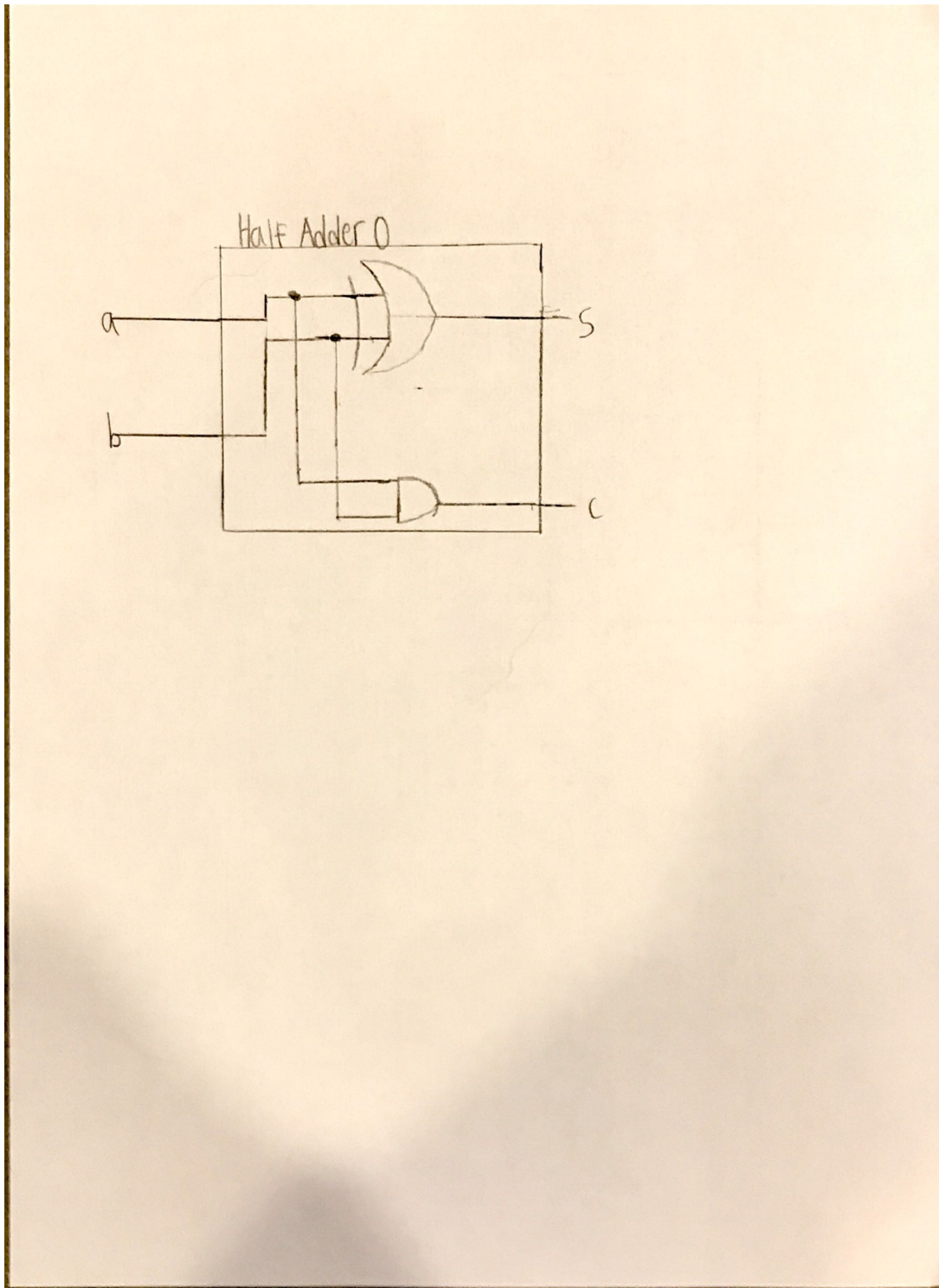


Figure 1: Block Diagram of the Half Adder

Time (ns):	0	10	20	30
a	0	1	0	1
b	0	0	1	1
c	0	0	0	1
s	0	1	1	0

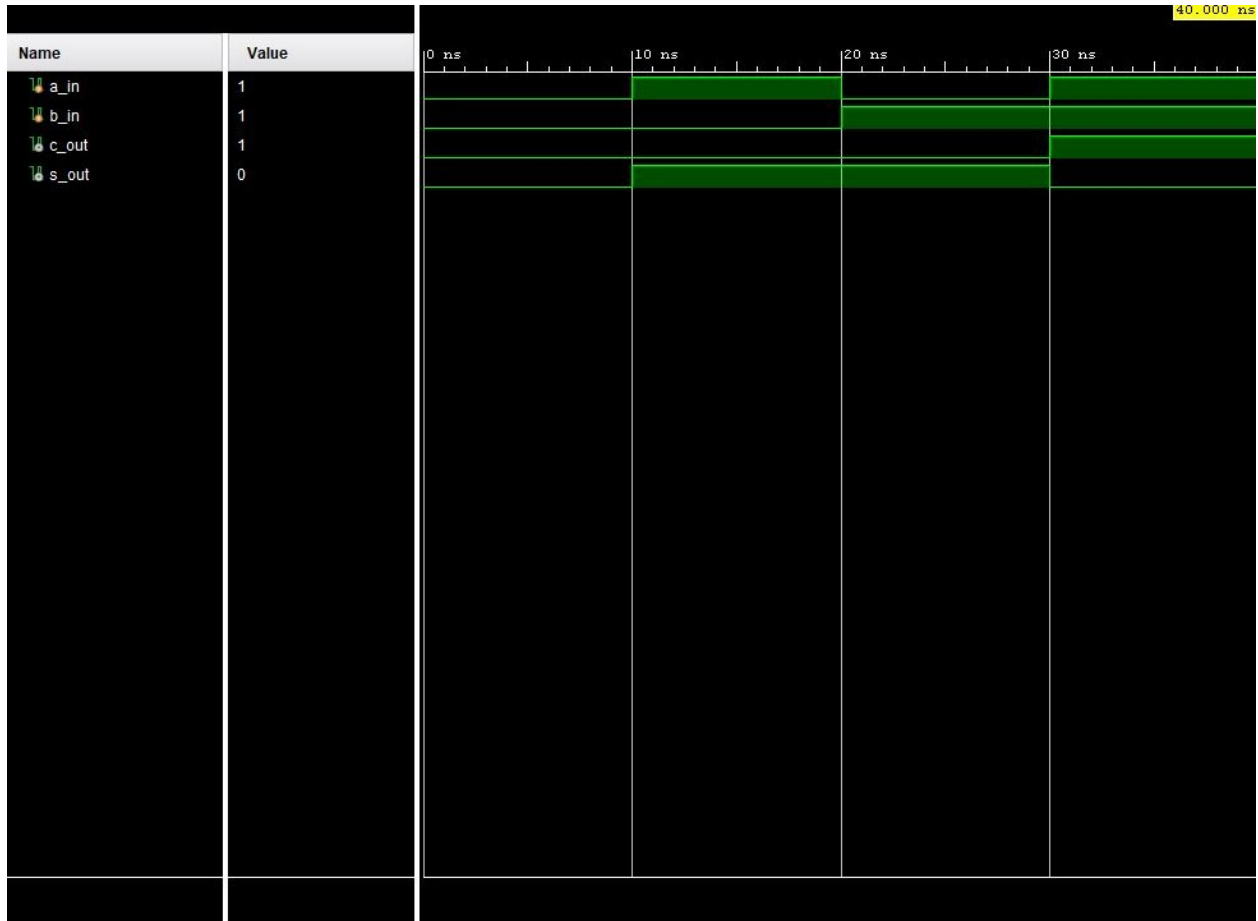


Figure 2: Half Adder simulation waveform and ERT

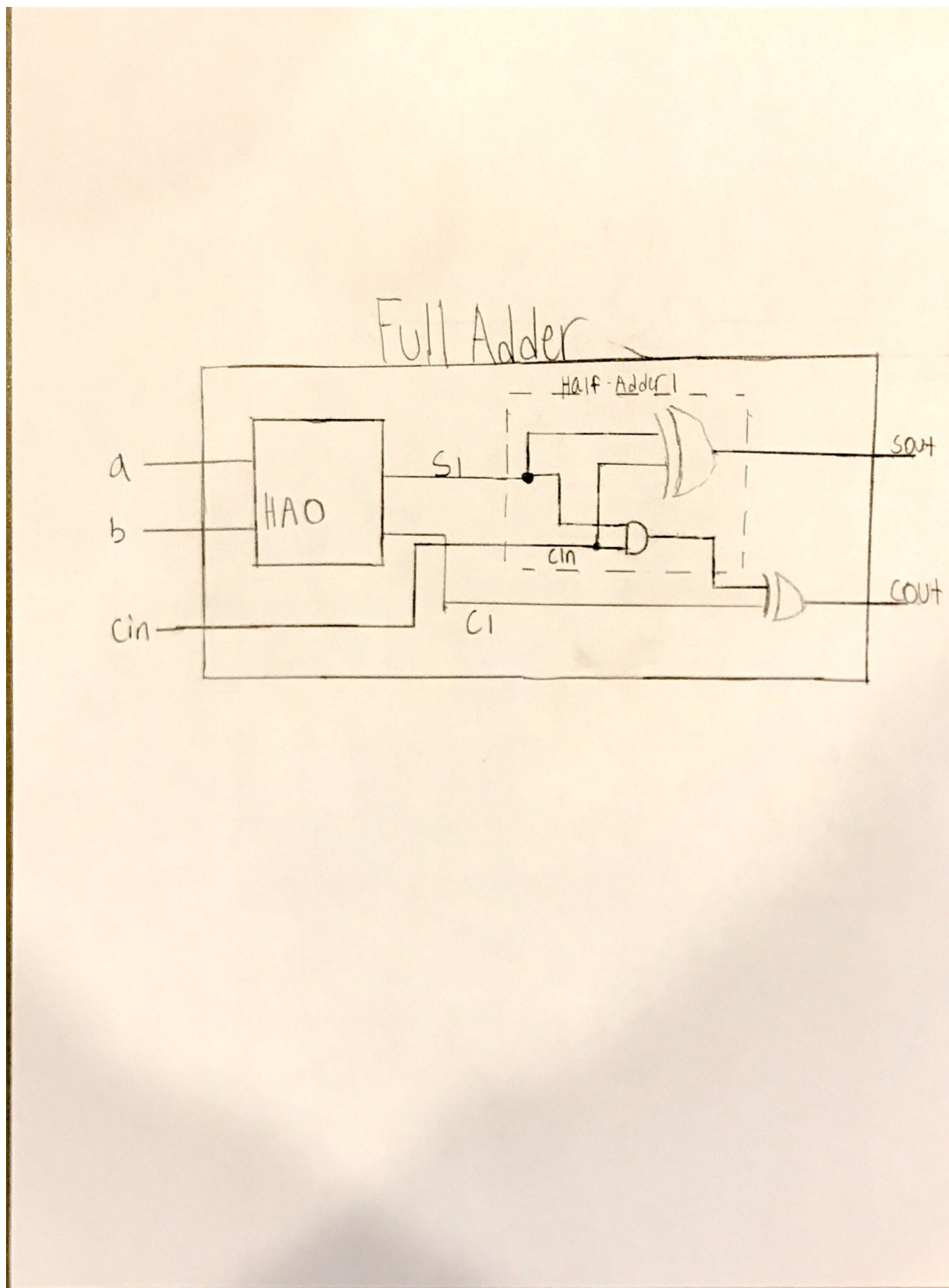


Figure 3: Block Diagram of Full Adder

Time (ns):	0	10	20	30	40	50	60	70
a	0	1	0	1	0	1	0	1
b	0	0	1	1	0	0	1	1
cin	0	0	0	0	1	1	1	1
c	0	0	0	1	0	1	1	1
s	0	1	1	0	1	0	0	1

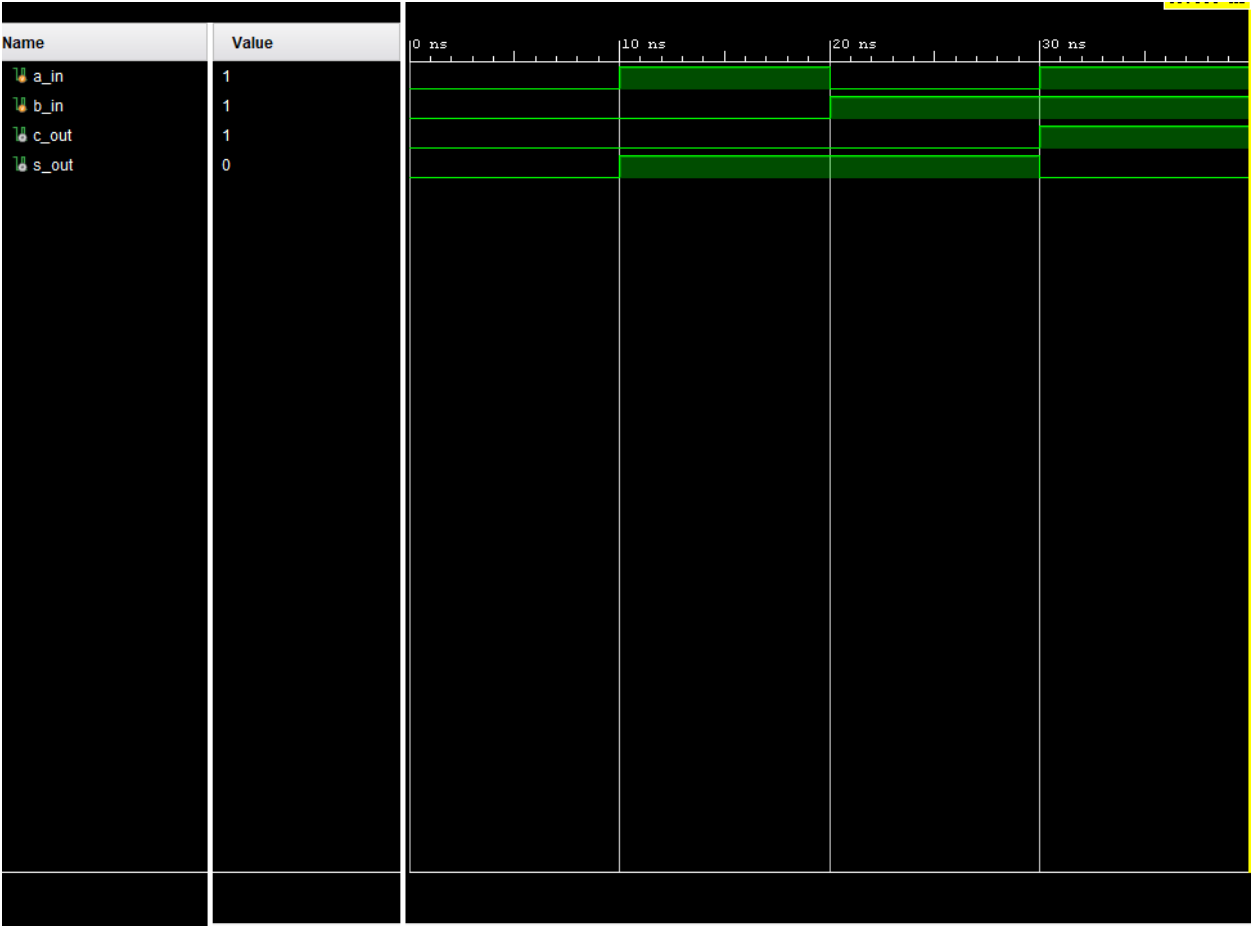


Figure 4: Full Adder simulation waveform and ERT

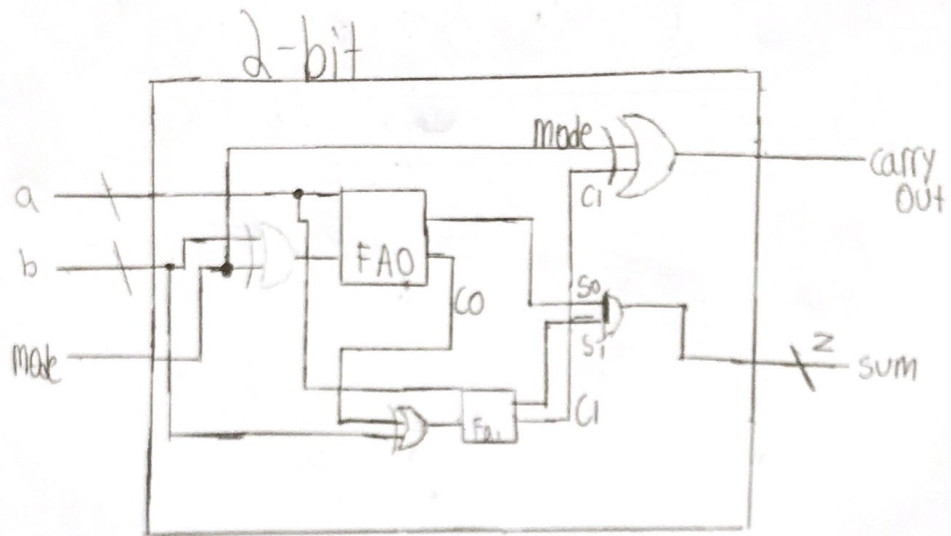


Figure 5: Block Diagram of 2 Bit Adder

Time (ns):	0	10	20	30	40	50	60	70	80	90	100	110	120	130
mode	1	1	1	1	1	1	1	0	0	0	0	0	0	0
a	00	00	00	00	01	10	10	00	00	00	00	01	10	10
b	00	01	10	11	01	01	00	00	01	10	11	01	01	00
c	0	1	1	1	0	0	0	0	0	0	0	0	0	0
s	00	11	10	01	00	01	10	00	01	10	11	10	11	10
deci	0	-1	-2	-3	0	1	2	0	1	2	3	2	3	2

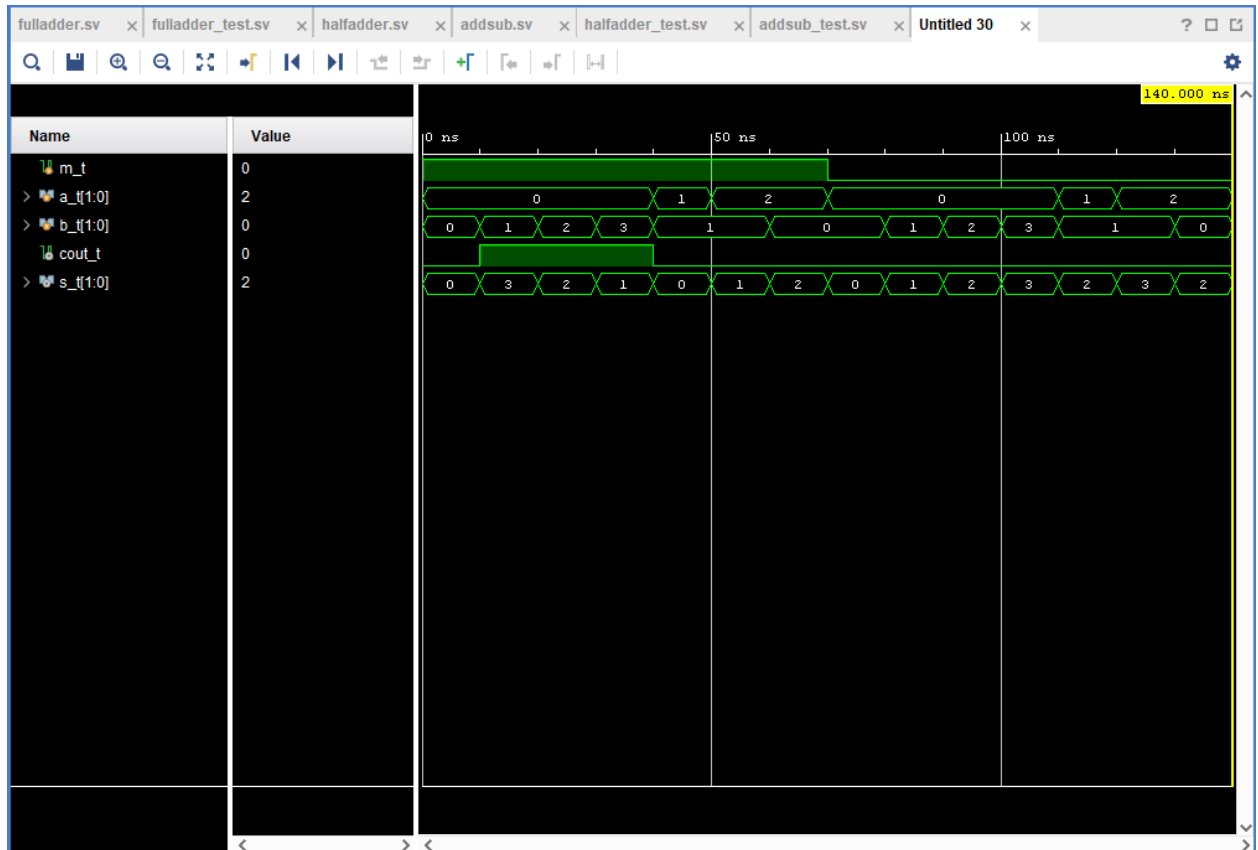


Figure 6: 2-Bit simulation waveform and ERT

The results match what was expected as the screenshotted waveform results confirm the expected results table.

Code

Listing 1: Half Adder Design Code

```
// Ashlie Lackey and CJ Jones , ELC 2137 , 2020 -2 -13
module halfadder ( input a , b ,
output s , c ) ;
// When using primitive instances , output is always the first port
xor (s , a , b ) ;
and (c , a , b ) ;
endmodule // halfadder
```

Listing 2: Half Adder Testbench Code

```
module example_and(
input a, b,
output c);
// c = a AND b
and(c,a,b);
endmodule
```

Listing 3: Full Adder Design Code

```
// Ashlie Lackey and CJ Jones , ELC 2137 , 2020 -2 -13
module fulladder (
input ain , bin , cin ,
output cout , sout
) ;

// Internal signals
wire c1 , c2 , s1 ;
// One instance of halfadder
halfadder ha0 (
. a ( ain ) , . b ( bin ) ,
. c ( c1 ) , . s ( s1 )
) ;
// second halfadder
halfadder ha1 (
. a ( s1 ) , . b ( cin ) ,
. c ( c2 ) , . s ( sout )
) ;

// Define carry output
xor (cout , c1 , c2 ) ;
endmodule // fulladder
```

Listing 4: Full Adder Testbench Code

```
// Ashlie Lackey and CJ Jones , ELC 2137 , 2020 -2 -13
module fulladder_test () ;
reg cin_t , a_t , b_t ;
wire cout_t , s_t ;
```

```

//instantiate fulladder
fulladder FA ( . ain ( a_t ) , . bin ( b_t ) , . cin ( cin_t ) , . sout (
    s_t ), . cout (cout_t) ) ;
// module here

initial begin
cin_t =0; a_t =0; b_t =0; #10;
//case2
{ a_t , b_t, cin_t } = 3'b100 ; #10;
//case3
{ a_t , b_t, cin_t } = 3'b010 ; #10;
//case4
{ a_t , b_t, cin_t } = 3'b110 ; #10;
//case5
{ a_t , b_t, cin_t } = 3'b001 ; #10;
//case6
{ a_t , b_t, cin_t } = 3'b101 ; #10;
//case7
{ a_t , b_t, cin_t } = 3'b011 ; #10;
//case8
{ a_t , b_t, cin_t } = 3'b111 ; #10;

$finish ;
end

endmodule // fulladder_test

```

Listing 5: 2-bit Adder Design Code

```

// Ashlie and CJ , ELC 2137 , 2020 -2 -13
module addsub (
input [1:0] a , b ,
input mode ,
output [1:0] sum ,
output cbout
) ;
// Internal signals
wire c1 , c2 ;
wire [1:0] b_n ;
// Invert b input for subtraction
assign b_n[0] = b[0] ^ mode;
assign b_n[1] = b[1] ^ mode;
//first full adder
fulladder fa0 (
. ain ( a [0] ) , . bin ( b_n [0] ) , . cin (
mode) ,
. cout ( c1 ) , . sout ( sum [0])
) ;
//second full adder
fulladder fa1 (
. ain ( a [1] ) , . bin ( b_n [1] ) , . cin (
c1 ) ,
. cout ( c2 ) , . sout ( sum [1])
) ;

```

```

// Convert carry to borrow when
// subtracting
assign cbout = c2 ^ mode;
endmodule // addsub

```

Listing 6: 2-bit Adder Testbench Code

```

// Ashlie Lackey , ELC 2137 , 2020 -2 -19
module addsub_test () ;
reg m_t;
reg [1:0] a_t, b_t;
wire cout_t ;
wire [1:0] s_t ;
// instantiate adder/subtractor
addsub AS(. a ( a_t ) , . b ( b_t ) , . mode ( m_t ) , . sum ( s_t ), .
    cbout (cout_t) ) ;
// module here

initial begin
//Subtraction Cases
//case1
{ a_t[1], b_t[1], a_t[0], b_t[0], m_t } = 5'b00001 ; #10;
//case2
{ a_t[1], b_t[1], a_t[0], b_t[0], m_t } = 5'b00011 ; #10;
//case3
{ a_t[1], b_t[1], a_t[0], b_t[0], m_t } = 5'b01001 ; #10;
//case4
{ a_t[1], b_t[1], a_t[0], b_t[0], m_t } = 5'b01011 ; #10;
//case5
{ a_t[1], b_t[1], a_t[0], b_t[0], m_t } = 5'b00111 ; #10;
//case6
{ a_t[1], b_t[1], a_t[0], b_t[0], m_t } = 5'b10011 ; #10;
//case7
{ a_t[1], b_t[1], a_t[0], b_t[0], m_t } = 5'b10001 ; #10;

//Addition Cases
//case8
{ a_t[1], b_t[1], a_t[0], b_t[0], m_t } = 5'b00000 ; #10;
//case9
{ a_t[1], b_t[1], a_t[0], b_t[0], m_t } = 5'b00010 ; #10;
//case10
{ a_t[1], b_t[1], a_t[0], b_t[0], m_t } = 5'b01000 ; #10;
//case11
{ a_t[1], b_t[1], a_t[0], b_t[0], m_t } = 5'b01010 ; #10;
//case12
{ a_t[1], b_t[1], a_t[0], b_t[0], m_t } = 5'b00110 ; #10;
//case13
{ a_t[1], b_t[1], a_t[0], b_t[0], m_t } = 5'b10010 ; #10;
//case14
{ a_t[1], b_t[1], a_t[0], b_t[0], m_t } = 5'b10000 ; #10;

$finish ;

```

```
end  
endmodule // addsub_test
```
