
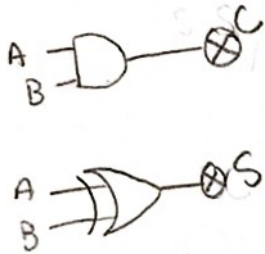


Circuit Demonstration Page


Half adder schematic

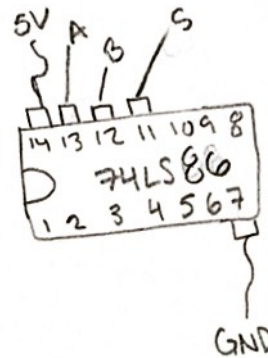


Half adder wiring diagram




Half adder: DR

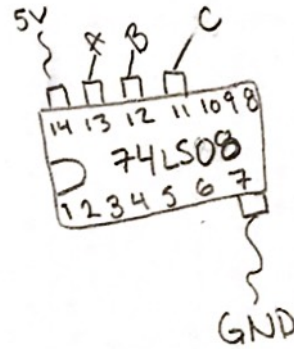


Full adder schematic

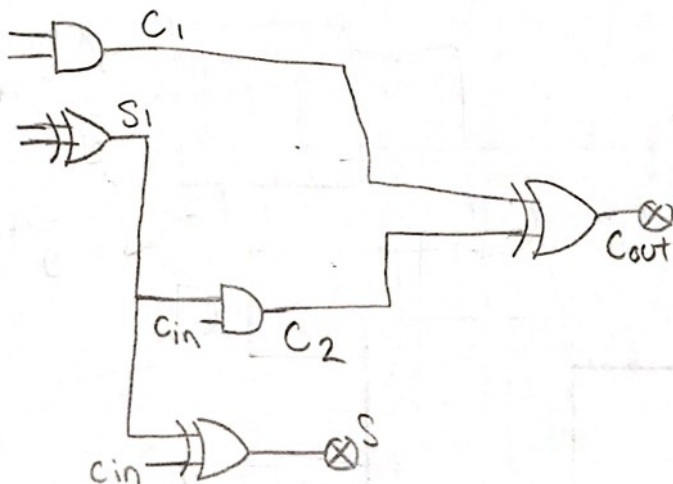

Full adder wiring diagram

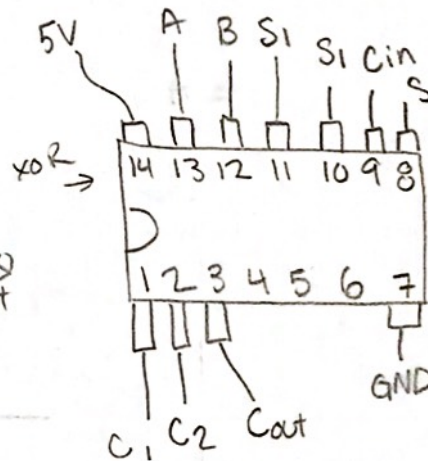

Full adder: DR

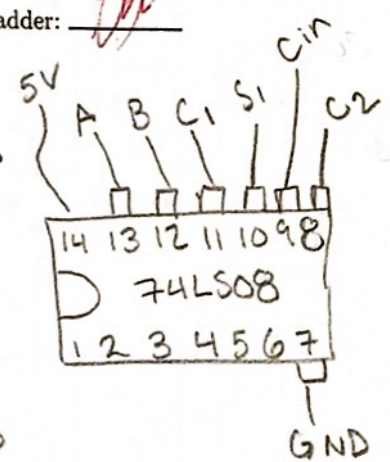

2-bit adder: DR