

ELC 2137 Lab 6: MUX and 7-segment Decoder

CJ Jones, Ashlie Lackey

February 27, 2020

Summary

This lab explored using a Basys3 board to produce an 8-bit number on a 7-segment display through a MUX combinational logic design. The MUX used had two inputs that were four bits each. Using Verilog, some skills gained in this lab include: writing a multiplexer utilizing the conditional operator, using always block, using multi-bit signals, producing a toplevel module, using constraint files, and creating a design on a FPGA board. Overall, this lab demonstrated how to utilize software and programmable logic to produce a hardware output.

Q&A

1. How many wires are connected to the 7-segment display?

The current seven segment display includes two 7-segment displays, so in total we used 10 wires. This is because the only wires we are "adding" in our current method are the anode wires while the segments are connected, effectively, across and don't provide any additional wires. Thus we have 8 wires that take care of all the segments, and 2 anodes for each separate digit display, making 10 in total.

2. If the segments were not all connected together, how many wires would there have to be?

If the segments were not all connected together, there would have to be separate wire systems for each individual 7-segment display. For the two (out of four) display numbers we used, each display would need 9 wires, totalling to 18 wires in total. Each display would have 8 wires for each segment, and the dp, and a wire for its anode, totalling to 9 per individual display, 18 all together.

3. Why do we prefer the current method vs. separating all of the segments?

We prefer the current method because it uses less wires. As the circuits become larger, the displays can only account for so many wires before it becomes egregiously expensive, and/or the chip breaks because of heating issues. Therefore, in using our current display for production, less wires means a cheaper circuit that is safer (less likely to fry), thus allowing for more displays to safely be possible. Therefore, the current method is preferred.

Results

Below are the Verilog source files (one for the MUX, 7-segment decoder, and the top-level module, along with their testbenches). Along with this are expected results tables for every testbench, and pictures of the Basys3 board displaying values on the two-different displays. Finally, a list of errors we encountered during our testbench modules include:

- 1.
- 2.
- 3.

This tells us in running simulations...

Time (ns):	0	10	20	30
in 0	0000	0001	0010	0010
in 1	0001	0010	0001	0001
sel	0	1	0	1
out	0000	0010	0010	0001

 


Figure 1: MUX2-4B simulation waveform and ERT

Time (ns):	0	10	20	30	40	50	60	70	80	90	100	110	120	130	140	150
Input num (hex)	0	1	2	3	4	5	6	7	8	9	a	b	c	d	e	f
Output sseg (hex)	40	79	24	30	19	12	02	38	00	10	08	03	46	21	06	0e

 


Figure 2: sseg- Decoder simulation waveform and ERT

Time (ns):	0	10	20	30	40	50	60	70	80	90	100	110	120	130	140	150	160
Input sw [7:0] (hex)	0	1	1	21	21	c8	c8	D3	D3	3D	3D	F0	F0	0F	0F	A5	A5
Input sw [15] (hex)	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
Output sseg	40	79	40	79	08	00	08	03	21	21	0e	40	78	78	12	12	00



Figure 3: sseg1 simulation waveform and ERT

Code

Listing 1: mux2-4b Module Code

```
// Ashlie Lackey and Chris Jones , ELC 2137, 2020 -2-26

module mux2_4b(

input [3:0]in0,

input [3:0]in1,

input sel,

output [3:0]out

);

assign out = sel?in1:in0;

endmodule
```

Listing 2: MUX Testbench Code

```
// Ashlie Lackey and Chris Jones , ELC 2137, 2020 -2-26

module mux2_4b_test();

reg [3:0]in0_t, in1_t;

reg sel_t;

wire [3:0]out_t;
```

```
mux2_4b Mux(.in1(in1_t), .in0(in0_t), .sel(sel_t), .out(out_t));

initial begin
in0_t = 4'b0000;
in1_t = 4'b0001;
sel_t = 0;
#10;

in0_t = 4'b0001;
in1_t = 4'b0010;
sel_t = 1;
#10;

in0_t = 4'b0010;
in1_t = 4'b0001;
sel_t = 0;
#10;

in0_t = 4'b0010;
in1_t = 4'b0001;
sel_t = 1;
#10;

$finish ;

end

endmodule    //mux2_4b_test
```

Listing 3: sseg Decoder Module Code

```
// Ashlie Lackey and Chris Jones , ELC 2137, 2020 -2-26

module sseg_decoder (
    input [3:0] num,
    output reg [6:0] sseg
) ;

// 4 - bit to 7 - segment decode logic
// ( note : output is active low)

always @*
    case (num)
        4'h0 : sseg = 7'b1000000 ;

        4'h1 : sseg = 7'b1111001 ;

        4'h2 : sseg = 7'b0100100 ;

        4'h3 : sseg = 7'b0110000 ;

        4'h4 : sseg = 7'b0011001 ;

        4'h5 : sseg = 7'b0010010 ;

        4'h6 : sseg = 7'b0000010 ;

        4'h7 : sseg = 7'b1111000 ;

        4'h8 : sseg = 7'b0000000 ;
```

```

4'h9 : sseg = 7'b0010000 ;

4'hA : sseg = 7'b0001000 ;

4'hB : sseg = 7'b0000011 ;

4'hC : sseg = 7'b1000110 ;

4'hD : sseg = 7'b0100001 ;

4'hE : sseg = 7'b0000110 ;

4'hF : sseg = 7'b0001110 ;

endcase

endmodule

```

Listing 4: sseg Decoder Testbench Code

```

// Ashlie Lackey and Chris Jones , ELC 2137, 2020 -2-26

module sseg_decoder_test () ;

reg [3:0]num_t;

wire [6:0]sseg_t;

integer i ; // Declare loop variable

sseg_decoder Bobby (.num(num_t), .sseg(sseg_t));

initial begin

for ( i =0; i <=8'hF ; i = i +1) begin

```

```

num_t = i;

#10;

end

$finish ;

end

endmodule // sseg_decoder_test

```

Listing 5: Top-level Module Code

```

// Ashlie Lackey and Chris Jones , ELC 2137, 2020 -2-26

module sseg1(
input [15:0]sw,
output [3:0]an,
output [6:0]seg,
output dp
);
wire [3:0] keith;
assign an[1] = ~sw[15];
assign an[0] = sw[15];
assign an[3:2] = 2'b11;
assign dp = 1;
mux2_4b william (.in1(sw[7:4]), .in0(sw[3:0]), .sel(sw[15]), .out(keith));
sseg_decoder robert(.num(keith), .sseg(seg));
endmodule

```

Listing 6: Top Level Module Testbench Code

```

// Ashlie Lackey and Chris Jones , ELC 2137, 2020 -2-26

module sseg1_test();

reg [15:0] sw_t;

```

```

wire [3:0] an_t;

wire [6:0] seg_t;

wire dp_t;

sseg1 sally(.sw(sw_t),.an(an_t),.seg(seg_t),.dp(dp_t)
);

initial begin

// Initialize

sw_t = 16'h0000; #10;

// Test case 1

sw_t [7:0] = 00000001;

sw_t [15] = 1'b0 ; #10;

sw_t [15] = 1'b1 ; #10;

// Test case 2

sw_t [7:0] = 00100001;

sw_t [15] = 1'b0 ; #10;

sw_t [15] = 1'b1 ; #10;

// Test case 3

sw_t [7:0] = 11001000;

sw_t [15] = 1'b0 ; #10;

sw_t [15] = 1'b1 ; #10;

// Test case 4

sw_t [7:0] = 11010011;

sw_t [15] = 1'b0 ; #10;

sw_t [15] = 1'b1 ; #10;

// Test case 5

sw_t [7:0] = 00111101;

```



```
sw_t [15] = 1'b0 ; #10;
sw_t [15] = 1'b1 ; #10;

// Test case 6
sw_t [7:0] = 11110000;
sw_t [15] = 1'b0 ; #10;
sw_t [15] = 1'b1 ; #10;

// Test case 7
sw_t [7:0] = 00001111;
sw_t [15] = 1'b0 ; #10;
sw_t [15] = 1'b1 ; #10;

// Test case 8
sw_t [7:0] = 10100101;
sw_t [15] = 1'b0 ; #10;
sw_t [15] = 1'b1 ; #10;

$finish;

end

endmodule
```
